

* Synchronous finite state machine specification:
Repetitive state order: 2, 7, 13, 6, 12, 14, 4, 3, 8, 1, 10,
Z active on state: 7.

* Asynchronous finite state machine specification:
Lock sequence: 5, 2, 4, 1, 9.

- ① state diagram ② state table ③ code assignment ④ transition table ⑤ K-map
⑥ minimised transition table ⑦ force it into not-allowed state
⑧ inclusion of transition equations assuming D-type flip-flops

~~Moore model finite state machine~~



2)

Synchronous

Output active on state 7.
Order of allowed states: 2, 7, 13, 6, 12, 14, 4,
3, 8, 1, 10, 5

Assume there are 16 states in total. Then unallocated states are 0, 9, 11, 15.

State diagram:

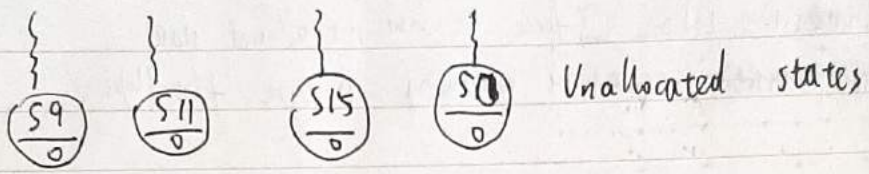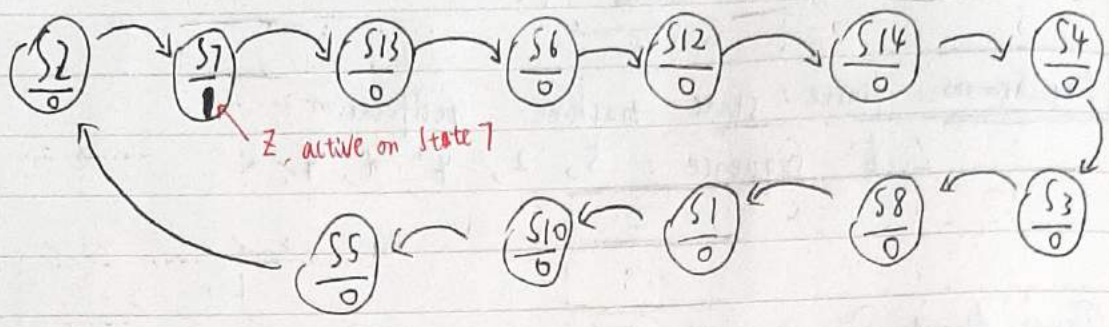

State table:

Present state	Next State	Present Output
S2	S7	0
S7	S13	1
S13	S6	0
S6	S12	0
S12	S14	0
S14	S4	0
S4	S3	0
S3	S8	0
S8	S1	0
S1	S10	0
S10	S5	0
S5	S2	0
S9	?	0
S11	?	0
S15	?	0
S0	?	0

Assign binary Gray code to each of these states.

State	Assigned code			
	Q_d	Q_c	Q_b	Q_a
S0	0	0	0	0
S1	0	0	0	1
S2	0	0	1	1
S3	0	0	1	0
S4	0	1	1	0
S5	0	1	1	1
S6	0	1	0	1
S7	0	1	0	0
S8	1	1	0	0
S9	1	1	0	1
S10	1	1	1	1
S11	1	1	1	0
S12	1	0	1	0
S13	1	0	1	1
S14	1	0	0	1
S15	1	0	0	0

Q_d Q_c Q_b Q_a Q_e



Assigned code Bits

Output Bit

We can reduce the code to four bits.

Present Time		Future time
D_n	Q_n	Q_{n+1}
0	0	0
0	1	0
1	0	1
1	1	1

Full-Form Transition Table of D-type

D-type flip-flops will be used in this assignment.

4)

The transition table can be derived: (ordered by specification)

Current State					Next State					D-Inputs				Z
State	Q_d	Q_c	Q_b	Q_a	State	Q_d	Q_c	Q_b	Q_a	D_d	D_c	D_b	D_a	
S2	0	0	1	1	S7	0	1	0	0	0	1	0	0	
S7	0	1	0	0	S13	1	0	1	1	1	0	1	1	1
S13	1	0	1	1	S6	0	1	0	1	0	1	0	1	
S6	0	1	0	1	S12	1	0	1	0	1	0	1	0	
S12	1	0	1	0	S14	1	0	0	1	1	0	0	1	
S14	1	0	0	1	S4	0	1	1	0	0	1	1	0	
S4	0	1	1	0	S3	0	0	1	0	0	0	1	0	
S3	0	0	1	0	S8	1	1	0	0	1	1	0	0	
S8	1	1	0	0	S1	0	0	0	1	0	0	0	1	
S1	0	0	0	1	S10	1	1	1	1	1	1	1	1	
S10	1	1	1	1	S5	0	1	1	1	0	1	1	1	
S5	0	1	1	1	S2	0	0	1	1	0	0	1	1	
S0	0	0	0	0	?	W_d	W_c	W_b	W_a	W_d	W_c	W_b	W_a	
S9	1	1	0	1	?	X_d	X_c	X_b	X_a	X_d	X_c	X_b	X_a	
S11	1	1	1	0	?	Y_d	Y_c	Y_b	Y_a	Y_d	Y_c	Y_b	Y_a	
S15	1	0	0	0	?	Z_d	Z_c	Z_b	Z_a	Z_d	Z_c	Z_b	Z_a	

z active on S7, $z = \bar{Q}_d \bar{Q}_c \bar{Q}_b \bar{Q}_a$

K-maps:

		Q_b, Q_a			
		00	01	11	10
Q_d, Q_c	00	W_a	1		
	01	1		1	
	11	1	X_a	1	Y_a
	10	Z_a		1	1

		Q_b, Q_a			
		00	01	11	10
Q_d, Q_c	00	W_b	1		
	01	1	1		1
	11		X_b	1	Y_b
	10	Z_b	1		

Transition Logic for D_a

Transition Logic for D_b

		Q_b, Q_a			
		00	01	11	10
Q_d, Q_c	00	W_c	1	1	1
	01				
	11		X_c	1	Y_c
	10	Z_c	1	1	

		Q_b, Q_a			
		00	01	11	10
Q_d, Q_c	00	W_d	1		1
	01	1	1		
	11		X_d		Y_d
	10	Z_d			1

Transition Logic for D_c

Transition Logic for D_d

According to above, we can get

$S0 \rightarrow W_a W_c W_b W_a = 1111$, corresponding to $S10$ which is an allowed state.

$S9 \rightarrow X_d X_c X_b X_a = 0110$, corresponding to $S4$ which is allowed.

$S11 \rightarrow Y_d Y_c Y_b Y_a = 0011$, corresponding to $S2$ which is allowed.

$S15 \rightarrow Z_d Z_c Z_b Z_a = 1001$, corresponding to $S14$ which is allowed.

Then we can confirm the design can satisfy the specification.

$$D_a = \bar{Q}_b \bar{Q}_a + \bar{Q}_d \bar{Q}_c \bar{Q}_b + Q_c Q_b Q_a + Q_d Q_b$$



$$D_b = \bar{Q}_d \bar{Q}_b + \bar{Q}_b Q_a + Q_c Q_b$$

$$D_c = \bar{Q}_d \bar{Q}_c + Q_d Q_a$$

$$D_d = \bar{Q}_d \bar{Q}_b + \bar{Q}_c \bar{Q}_a$$

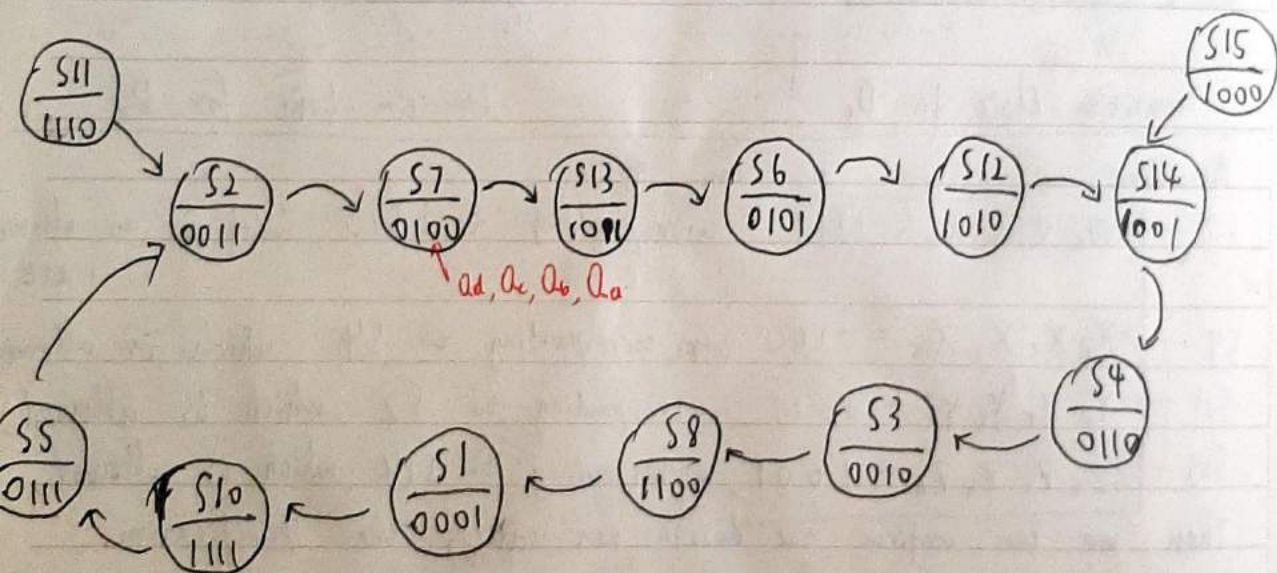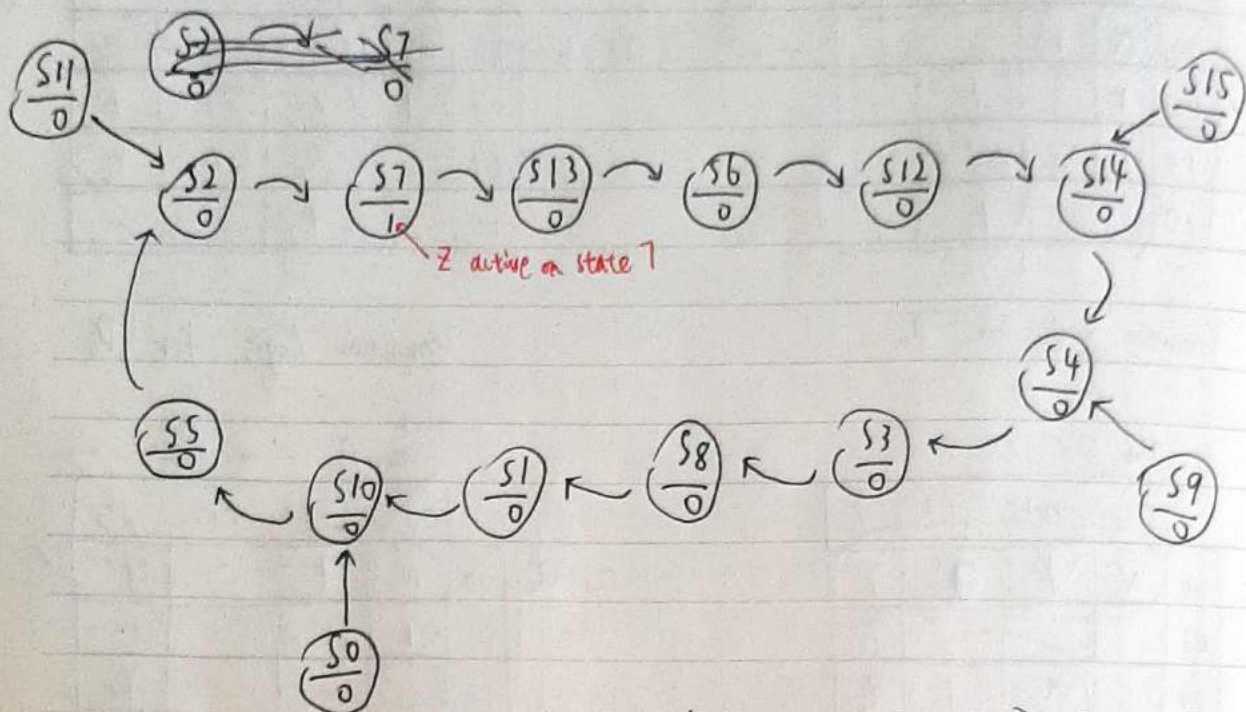6)

Re-draw the final state ~~Diagram~~ Diagram:



Final transition Table :

Current State					Next State					Next D-Inputs				Z
State	Q _d	Q _c	Q _b	Q _a	State	Q _d	Q _c	Q _b	Q _a	D _d	D _c	D _b	D _a	0
S2	0	0	1	1	S7	0	1	0	0	0	1	0	0	0
S7	0	1	0	0	S13	1	0	1	1	1	0	1	1	1
S13	1	0	1	1	S6	0	1	0	1	0	1	0	1	0
S6	0	1	0	1	S12	1	0	1	0	1	0	1	0	0
S12	1	0	1	0	S14	1	0	0	1	1	0	0	1	0
S14	1	0	0	1	S4	0	1	1	0	0	1	1	0	0
S4	0	1	1	0	S3	0	0	1	0	0	0	1	0	0
S3	0	0	1	0	S8	1	1	0	0	1	1	0	0	0
S8	1	1	0	0	S1	0	0	0	1	0	0	0	1	0
S1	0	0	0	1	S10	1	1	1	1	1	1	1	1	0
S10	1	1	1	1	S5	0	1	1	1	0	1	1	1	0
S5	0	1	1	1	S2	0	0	1	1	0	0	1	1	0
S0	0	0	0	0	S10	1	1	1	1	1	1	1	1	0
S9	1	1	0	1	S4	0	1	1	0	0	1	1	0	0
S11	1	1	1	0	S2	0	0	1	1	0	0	1	1	0
S15	1	0	0	0	S14	1	0	0	1	1	0	0	1	0

Asynchronous

Key 1	Key 2	Key 3	Key 4	Key 5
5	2	4	1	9

State Diagram:


First, we should define some pre-processed functions. As the five-digit code sequence is 5, 2, 4, 1, 9 in specification, the pre-processed functions are as following:

k_x : represent key number 5 pressed and no other key

k_x : represent key number X (0~9) pressed and no other key.

\hat{k}_x : represent any key other than key X, or a combination of keys pressed.

[0]: represent no keys pressed

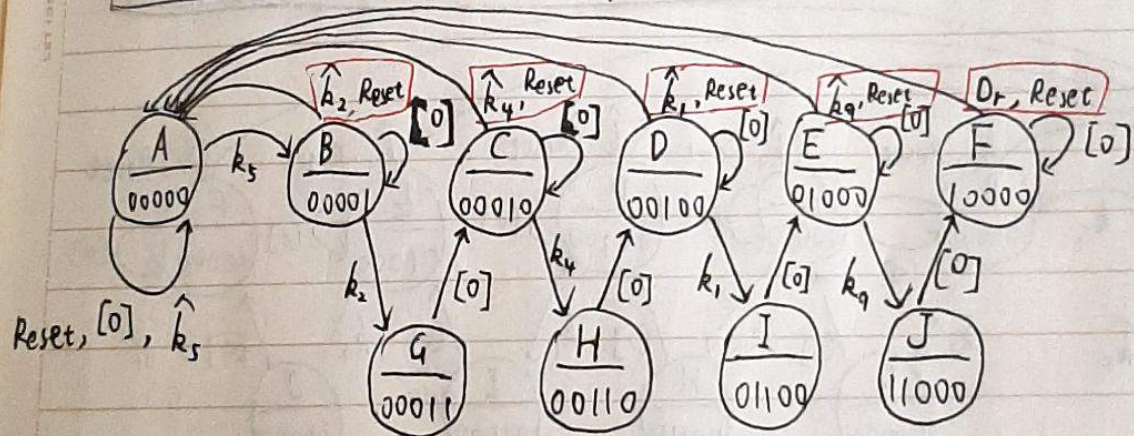


In order to add fraud-protection transitions and avoid race hazards, we use one-hot code ~~str~~ and ~~two-hot~~ two-hot code strategy to assign states.

Code Assignment :

State	Q_e	Q_d	Q_c	Q_b	Q_a	Z
A	0	0	0	0	0	0
B	0	0	0	0	1	0
C	0	0	0	1	0	0
D	0	0	1	0	0	0
E	0	1	0	0	0	0
F	1	0	0	0	0	1
G	0	0	0	1	1	0
H	0	0	1	1	0	0
I	0	1	1	0	0	0
J	1	1	0	0	0	0

Lock sequence: 52419

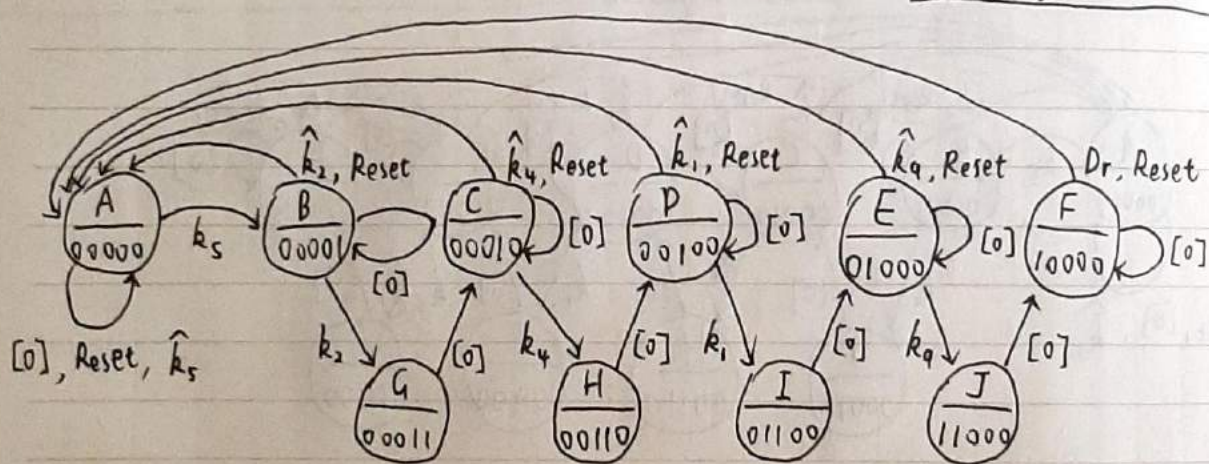

Transition Table

Present State																	Next State										
State	Q _e	Q _d	Q _c	Q _b	Q _a	Reset	[0]	k ₅	k̂ ₅	k ₄	k̂ ₄	k ₃	k̂ ₃	k ₂	k̂ ₂	k ₁	k̂ ₁	k ₀	k̂ ₀	Dr	State	Q _e	Q _d	Q _c	Q _b	Q _a	
A	0	0	0	0	0	1																A	0	0	0	0	0
A	0	0	0	0	0		1															A	0	0	0	0	0
A	0	0	0	0	0			1														B	0	0	0	0	1
A	0	0	0	0	0				1													A	0	0	0	0	0
B	0	0	0	0	1	1																A	0	0	0	0	0
B	0	0	0	0	1		1															B	0	0	0	0	1
B	0	0	0	0	1						1											G	0	0	0	1	1
B	0	0	0	0	1							1										A	0	0	0	0	0
C	0	0	0	1	0	1																A	0	0	0	0	0
C	0	0	0	1	0		1															C	0	0	0	1	0
C	0	0	0	1	0								1									H	0	0	1	1	0
C	0	0	0	1	0									1								A	0	0	0	0	0
D	0	0	1	0	0	1																A	0	0	0	0	0
D	0	0	1	0	0		1															D	0	0	1	0	0
D	0	0	1	0	0													1				I	0	1	1	0	0
D	0	0	1	0	0														1			A	0	0	0	0	0
E	0	1	0	0	0	1																A	0	0	0	0	0
E	0	1	0	0	0		1															E	0	1	0	0	0
E	0	1	0	0	0															1		J	1	1	0	0	0
E	0	1	0	0	0																1	A	0	0	0	0	0
F	1	0	0	0	0	1																A	0	0	0	0	0
F	1	0	0	0	0		1															F	1	0	0	0	0
F	1	0	0	0	0																1	A	0	0	0	0	0
G	0	0	0	1	1		1															C	0	0	0	1	0
H	0	0	1	1	0		1															D	0	0	1	0	0
I	0	1	1	0	0		1															E	0	1	0	0	0
J	1	1	0	0	0		1															F	1	0	0	0	0

Expand the pre-processed functions:

$$[0] = \overline{k_0} \overline{k_1} \overline{k_2} \overline{k_3} \overline{k_4} \overline{k_5} \overline{k_6} \overline{k_7} \overline{k_8} \overline{k_9}$$

$$k_5 = \overline{k_0} \overline{k_1} \overline{k_2} \overline{k_3} \overline{k_4} k_5 \overline{k_6} \overline{k_7} \overline{k_8} \overline{k_9}$$

$$\hat{k}_5 = \overline{k_0} \overline{k_1} \overline{k_2} \overline{k_3} \overline{k_4} k_5 \overline{k_6} \overline{k_7} \overline{k_8} \overline{k_9}$$

$$k_2 = \overline{k_0} \overline{k_1} k_2 \overline{k_3} \overline{k_4} \overline{k_5} \overline{k_6} \overline{k_7} \overline{k_8} \overline{k_9}$$

$$\hat{k}_2 = \overline{k_0} \overline{k_1} k_2 \overline{k_3} \overline{k_4} \overline{k_5} \overline{k_6} \overline{k_7} \overline{k_8} \overline{k_9}$$

$$k_4 = \overline{k_0} \overline{k_1} \overline{k_2} \overline{k_3} k_4 \overline{k_5} \overline{k_6} \overline{k_7} \overline{k_8} \overline{k_9}$$

$$\hat{k}_4 = \overline{k_0} \overline{k_1} \overline{k_2} \overline{k_3} k_4 \overline{k_5} \overline{k_6} \overline{k_7} \overline{k_8} \overline{k_9}$$

$$k_1 = \overline{k_0} k_1 \overline{k_2} \overline{k_3} \overline{k_4} \overline{k_5} \overline{k_6} \overline{k_7} \overline{k_8} \overline{k_9}$$

$$\hat{k}_1 = \overline{k_0} k_1 \overline{k_2} \overline{k_3} \overline{k_4} \overline{k_5} \overline{k_6} \overline{k_7} \overline{k_8} \overline{k_9}$$

$$k_9 = \overline{k_0} \overline{k_1} \overline{k_2} \overline{k_3} \overline{k_4} \overline{k_5} \overline{k_6} \overline{k_7} \overline{k_8} k_9$$

$$\hat{k}_9 = \overline{k_0} \overline{k_1} \overline{k_2} \overline{k_3} \overline{k_4} \overline{k_5} \overline{k_6} \overline{k_7} \overline{k_8} k_9$$

$$[0] = \overline{k_0} \overline{k_1} \overline{k_2} \overline{k_3} \overline{k_4} \overline{k_5} \overline{k_6} \overline{k_7} \overline{k_8} \overline{k_9}$$

Note: Ten keys on key board

$$Q_a = \bar{Q}_e \bar{Q}_d \bar{Q}_c \bar{Q}_b \bar{Q}_a k_5 + \bar{Q}_e \bar{Q}_d \bar{Q}_c \bar{Q}_b Q_a [0] + \bar{Q}_e \bar{Q}_d \bar{Q}_c \bar{Q}_b Q_a k_9$$

$$= \bar{Q}_e \bar{Q}_d \bar{Q}_c \bar{Q}_b \bar{Q}_a \bar{k}_0 \bar{k}_1 \bar{k}_2 \bar{k}_3 \bar{k}_4 k_5 k_6 \bar{k}_7 \bar{k}_8 \bar{k}_9$$

$$+ \bar{Q}_e \bar{Q}_d \bar{Q}_c \bar{Q}_b Q_a \bar{k}_0 \bar{k}_1 \bar{k}_2 \bar{k}_3 \bar{k}_4 k_5 k_6 \bar{k}_7 \bar{k}_8 \bar{k}_9$$

$$+ \bar{Q}_e \bar{Q}_d \bar{Q}_c \bar{Q}_b Q_a \bar{k}_0 \bar{k}_1 k_2 \bar{k}_3 \bar{k}_4 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8 \bar{k}_9$$

$$Q_b = \bar{a}_e \bar{a}_d \bar{a}_c \bar{a}_b a_a k_2 + \bar{a}_e \bar{a}_d \bar{a}_c a_b \bar{a}_a k_4 + \bar{a}_e \bar{a}_d \bar{a}_c a_b \bar{a}_a [0] \\ + \bar{a}_e \bar{a}_d \bar{a}_c a_b a_a [0] \\ = \bar{a}_e \bar{a}_d \bar{a}_c \bar{a}_b a_a \bar{k}_0 \bar{k}_1 k_2 \bar{k}_3 \bar{k}_4 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8 \bar{k}_9 \\ + \bar{a}_e \bar{a}_d \bar{a}_c a_b \bar{a}_a \bar{k}_0 \bar{k}_1 \bar{k}_2 \bar{k}_3 k_4 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8 \bar{k}_9 \\ + \bar{a}_e \bar{a}_d \bar{a}_c a_b \bar{a}_a \bar{k}_0 \bar{k}_1 \bar{k}_2 \bar{k}_3 \bar{k}_4 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8 \bar{k}_9 \\ + \bar{a}_e \bar{a}_d \bar{a}_c a_b a_a \bar{k}_0 \bar{k}_1 \bar{k}_2 \bar{k}_3 \bar{k}_4 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8 \bar{k}_9$$

$$Q_c = \bar{Q}_e \bar{Q}_d \bar{Q}_c Q_b \bar{Q}_a k_4 + \bar{Q}_e \bar{Q}_d Q_c \bar{Q}_b \bar{Q}_a [0] + \bar{Q}_e \bar{Q}_d Q_c \bar{Q}_b \bar{Q}_a k_1 + \bar{Q}_e \bar{Q}_d Q_c Q_b \bar{Q}_a [0]$$

$$= \bar{Q}_e \bar{Q}_d \bar{Q}_c Q_b \bar{Q}_a \bar{k}_0 \bar{k}_1 \bar{k}_2 \bar{k}_3 k_4 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8 \bar{k}_9 + \bar{Q}_e \bar{Q}_d Q_c \bar{Q}_b \bar{Q}_a \bar{k}_0 \bar{k}_1 \bar{k}_2 \bar{k}_3 \bar{k}_4 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8 \bar{k}_9 + \bar{Q}_e \bar{Q}_d Q_c \bar{Q}_b \bar{Q}_a \bar{k}_0 k_1 \bar{k}_2 \bar{k}_3 \bar{k}_4 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8 \bar{k}_9 + \bar{Q}_e \bar{Q}_d Q_c Q_b \bar{Q}_a \bar{k}_0 \bar{k}_1 \bar{k}_2 \bar{k}_3 \bar{k}_4 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8 \bar{k}_9$$

$$Q_d = \bar{Q}_e \bar{Q}_d Q_c \bar{Q}_b \bar{Q}_a k_1 + \bar{Q}_e Q_d \bar{Q}_c \bar{Q}_b \bar{Q}_a [0] + \bar{Q}_e Q_d \bar{Q}_c \bar{Q}_b Q_a k_9$$

$$+ \bar{Q}_e Q_d Q_c \bar{Q}_b \bar{Q}_a [0]$$

$$= \bar{Q}_e \bar{Q}_d Q_c \bar{Q}_b \bar{Q}_a \bar{k}_0 \bar{k}_1 \bar{k}_2 \bar{k}_3 \bar{k}_4 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8 \bar{k}_9$$

$$+ \bar{Q}_e Q_d \bar{Q}_c \bar{Q}_b \bar{Q}_a \bar{k}_0 \bar{k}_1 \bar{k}_2 \bar{k}_3 \bar{k}_4 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8 \bar{k}_9$$

$$+ \bar{Q}_e Q_d \bar{Q}_c \bar{Q}_b Q_a \bar{k}_0 \bar{k}_1 \bar{k}_2 \bar{k}_3 \bar{k}_4 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8 \bar{k}_9$$

$$+ \bar{Q}_e Q_d Q_c \bar{Q}_b Q_a \bar{k}_0 \bar{k}_1 \bar{k}_2 \bar{k}_3 \bar{k}_4 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8 \bar{k}_9$$

$$\begin{aligned}
 Q_e &= \bar{Q}_e Q_d \bar{Q}_c \bar{Q}_b \bar{Q}_a k_9 + Q_e \bar{Q}_d \bar{Q}_c \bar{Q}_b \bar{Q}_a [0] + Q_e Q_d \bar{Q}_c \bar{Q}_b \bar{Q}_a [0] \\
 &= \bar{Q}_e Q_d \bar{Q}_c \bar{Q}_b \bar{Q}_a \bar{k}_0 \bar{k}_1 \bar{k}_2 \bar{k}_3 \bar{k}_4 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8 k_9 \\
 &\quad + Q_e \bar{Q}_d \bar{Q}_c \bar{Q}_b \bar{Q}_a \bar{k}_0 \bar{k}_1 \bar{k}_2 \bar{k}_3 \bar{k}_4 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8 \bar{k}_9 \\
 &\quad + Q_e Q_d \bar{Q}_c \bar{Q}_b \bar{Q}_a \bar{k}_0 \bar{k}_1 \bar{k}_2 \bar{k}_3 \bar{k}_4 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8 \bar{k}_9
 \end{aligned}$$

Extraction of Prime Implicants:

$Q_a = (\text{Common Variables}) \cdot (\text{Remaining Variables})$

$$\cancel{Q_a = \bar{Q}_e \bar{Q}_d \bar{Q}_c \bar{Q}_b \bar{Q}_a}$$

$$\begin{aligned}
 Q_a &= (\bar{Q}_e \bar{Q}_d \bar{Q}_c \bar{Q}_b \bar{k}_0 \bar{k}_1 \bar{k}_3 \bar{k}_4 \bar{k}_6 \bar{k}_7 \bar{k}_8 \bar{k}_9) (\bar{Q}_a k_5 + Q_a \bar{k}_5) \\
 &\quad \cdot (\bar{Q}_a \bar{k}_2 k_5 + Q_a \bar{k}_2 \bar{k}_5 + Q_a k_2 \bar{k}_5)
 \end{aligned}$$

$$\begin{aligned}
 Q_b &= (\bar{Q}_e \bar{Q}_d \bar{Q}_c \bar{k}_0 \bar{k}_1 \bar{k}_3 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8 \bar{k}_9) \\
 &\quad \cdot (\bar{Q}_b Q_a k_2 \bar{k}_4 + Q_b \bar{Q}_a \bar{k}_2 k_4 + Q_b \bar{Q}_a \bar{k}_2 \bar{k}_4 + Q_b Q_a \bar{k}_2 \bar{k}_4)
 \end{aligned}$$

$$\begin{aligned}
 Q_c &= (\bar{Q}_e \bar{Q}_d \bar{Q}_a \bar{k}_0 \bar{k}_2 \bar{k}_3 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8 \bar{k}_9) \\
 &\quad \cdot (\bar{Q}_c Q_b \bar{k}_1 k_4 + Q_c \bar{Q}_b \bar{k}_1 \bar{k}_4 + Q_c \bar{Q}_b k_1 \bar{k}_4 + Q_c Q_b \bar{k}_1 \bar{k}_4)
 \end{aligned}$$

$$\begin{aligned}
 Q_d &= (\bar{Q}_e \bar{Q}_b \bar{Q}_a \bar{k}_0 \bar{k}_2 \bar{k}_3 \bar{k}_4 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8) \\
 &\quad \cdot (\bar{Q}_d Q_c k_1 \bar{k}_9 + Q_d \bar{Q}_c \bar{k}_1 \bar{k}_9 + Q_d \bar{Q}_c k_1 k_9 + Q_d Q_c \bar{k}_1 \bar{k}_9)
 \end{aligned}$$

$$\cancel{Q_e = Q_c Q_b Q_a}$$

$$\begin{aligned}
 Q_e &= (\bar{Q}_c \bar{Q}_b \bar{Q}_a \bar{k}_0 \bar{k}_1 \bar{k}_2 \bar{k}_3 \bar{k}_4 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8) \\
 &\quad \cdot (\bar{Q}_e Q_d k_9 + Q_e \bar{Q}_d \bar{k}_9 + Q_e Q_d \bar{k}_9)
 \end{aligned}$$

k-maps of remaining variables:

Q _a	k ₂ k ₅			
	00	01	11	10
0		1		
1	1			1

Transition Logic for Q_a

Q _b Q _a	k ₂ k ₄			
	00	01	11	10
00				
01				1
11	1			
10	1	1		

Transition Logic for Q_b

Q _c Q _b	k ₁ k ₄			
	00	01	11	10
00				
01		1		
11	1			
10	1			1

Transition Logic for Q_c

Q _d Q _c	k ₁ k ₄			
	00	01	11	10
00				
01				1
11	1			
10	1	1		

Transition Logic for Q_d

Q _e	Q _d k ₉			
	00	01	11	10
0			1	
1	1			1

Transition Logic for Q_e

$$Q_a(\text{Remaining Variables}) = Q_a \bar{k}_5 + \bar{Q}_a \bar{k}_2 k_5$$

$$Q_b(\text{Remaining Variables}) = Q_b \bar{k}_2 \bar{k}_4 + Q_b \bar{Q}_a \bar{k}_2 + \bar{Q}_b Q_a k_2 \bar{k}_4$$

$$(\text{Remaining}) Q_c = Q_b \bar{k}_1 \bar{k}_4 + Q_c \bar{Q}_b \bar{k}_4$$

$$(\text{Remaining}) Q_d = Q_d \bar{Q}_c \bar{k}_1 + Q_d \bar{k}_1 \bar{k}_9 + \bar{Q}_d Q_c k_1 \bar{k}_9$$

$$(\text{Remaining}) Q_e = \bar{Q}_e Q_d k_9 + Q_e \bar{k}_9$$

$$(\text{Remaining}) Q_c = Q_c \bar{Q}_b \bar{k}_4 + Q_c \bar{k}_1 \bar{k}_4 + \bar{Q}_c Q_b \bar{k}_1 k_4$$

Then we can get:

(Common Variables) • (Remainning Variables)

$$Q_a = (\bar{Q}_e \bar{Q}_d \bar{Q}_c \bar{Q}_b \bar{k}_0 \bar{k}_1 \bar{k}_3 \bar{k}_4 \bar{k}_6 \bar{k}_7 \bar{k}_8 \bar{k}_9) \\ \cdot (\bar{Q}_a \bar{k}_2 \bar{k}_5 + \bar{Q}_a \bar{k}_2 k_5 + Q_a \bar{k}_5)$$

$$Q_b = (\bar{Q}_e \bar{Q}_d \bar{Q}_c \bar{k}_0 \bar{k}_1 \bar{k}_3 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8 \bar{k}_9) \\ \cdot (\bar{Q}_b Q_a k_2 \bar{k}_4 + Q_b \bar{Q}_a \bar{k}_2 + Q_b \bar{k}_2 \bar{k}_4)$$

$$Q_c = (\bar{Q}_e \bar{Q}_d \bar{Q}_a \bar{k}_0 \bar{k}_2 \bar{k}_3 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8 \bar{k}_9) \\ \cdot (\bar{Q}_c Q_b k_1 \bar{k}_4 + Q_c \bar{Q}_b \bar{k}_4 + Q_b \bar{k}_1 \bar{k}_4) \\ \cdot (Q_c \bar{Q}_b \bar{k}_4 + Q_c \bar{k}_1 \bar{k}_4 + \bar{Q}_c Q_b k_1 k_4)$$

$$Q_d = (\bar{Q}_e \bar{Q}_b \bar{Q}_a \bar{k}_0 \bar{k}_2 \bar{k}_3 \bar{k}_4 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8) \\ \cdot (Q_d \bar{Q}_c \bar{k}_1 + Q_d \bar{k}_1 \bar{k}_9 + \bar{Q}_d Q_c k_1 \bar{k}_9)$$

$$Q_e = (\bar{Q}_c \bar{Q}_b \bar{Q}_a \bar{k}_0 \bar{k}_1 \bar{k}_2 \bar{k}_3 \bar{k}_4 \bar{k}_5 \bar{k}_6 \bar{k}_7 \bar{k}_8) \\ \cdot (\bar{Q}_e Q_d k_9 + Q_e \bar{k}_9)$$

Removing common variables of all transition equations:

$$Q_a = (\bar{Q}_e \bar{Q}_d \bar{Q}_c \bar{Q}_b \bar{k}_1 \bar{k}_4 \bar{k}_9) \cdot (\bar{Q}_a \bar{k}_2 \bar{k}_5 + Q_a \bar{k}_5)$$


$$Q_b = (\bar{Q}_e \bar{Q}_d \bar{Q}_c \bar{k}_1 \bar{k}_5 \bar{k}_9) \cdot (\bar{Q}_b Q_a k_2 \bar{k}_4 + Q_b \bar{Q}_a \bar{k}_2 + Q_b \bar{k}_2 \bar{k}_4)$$

$$Q_c = (\bar{Q}_e \bar{Q}_d \bar{Q}_a \bar{k}_2 \bar{k}_5 \bar{k}_9) \cdot (\bar{Q}_c \bar{Q}_b \bar{k}_4 + Q_b \bar{k}_1 \bar{k}_4) \\ \cdot (Q_c \bar{Q}_b \bar{k}_4 + Q_c \bar{k}_1 \bar{k}_4 + \bar{Q}_c Q_b k_1 k_4)$$

$$Q_d = (\bar{Q}_e \bar{Q}_b \bar{Q}_a \bar{k}_2 \bar{k}_4 \bar{k}_5) \cdot (Q_d \bar{Q}_c \bar{k}_1 + Q_d \bar{k}_1 \bar{k}_9 + \bar{Q}_d Q_c k_1 \bar{k}_9)$$


$$Q_e = (\bar{Q}_c \bar{Q}_b \bar{Q}_a \bar{k}_1 \bar{k}_2 \bar{k}_4 \bar{k}_5) \cdot (\bar{Q}_e Q_d k_9 + Q_e \bar{k}_9)$$

Implementation: (Synchronous)

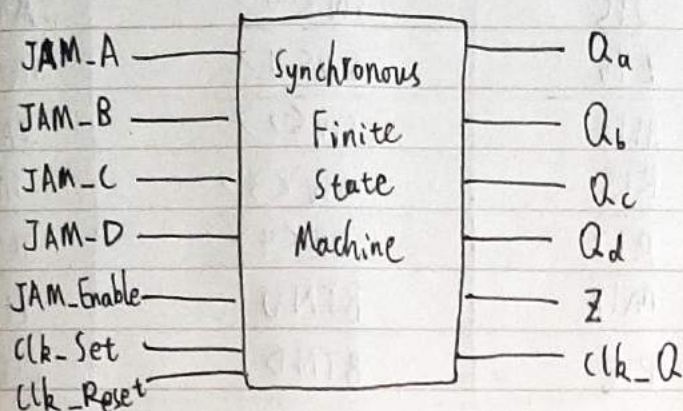

(Input)

(output)

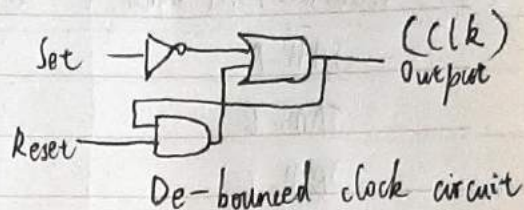


$$clk = \overline{Reset} + \overline{Set} \cdot clk$$

Editing the constraints files "Noxys-4-DDR-MSC-Fragment-1.xdc" and map the name of corresponding variables to pins as follows below.

(output) Synchronous FSM Signals	Artix-7 IO Pins	Original Digilent Net Name	Edited Digilent Net Name
Qa	H17	LED<0>	Qa
Qb	K15	LED<1>	Qb
Qc	J13	LED<2>	Qc
Qd	N14	LED<3>	Qd
Z	R18 V17	LED<5>	Z
clk_Q	V U16	LED<7>	clk_Q

(Input) Synchronous FSM Signal	Artix I/O Pins	Original Pin/Digit/Net Name	Edited Digit/Net Name
JAM-A	J15	SW<0>	JAM-A
JAM-B	L16	SW<1>	JAM-B
JAM-C	M13	SW<2>	JAM-C
JAM-D	R15	SW<3>	JAM-D
JAM-Enable	R17	SW<4>	JAM-Enable
clk-See	M18	BTNU	clk-See
clk-Reset	P18	BTND	clk-Reset

Implementation : (Asynchronous)

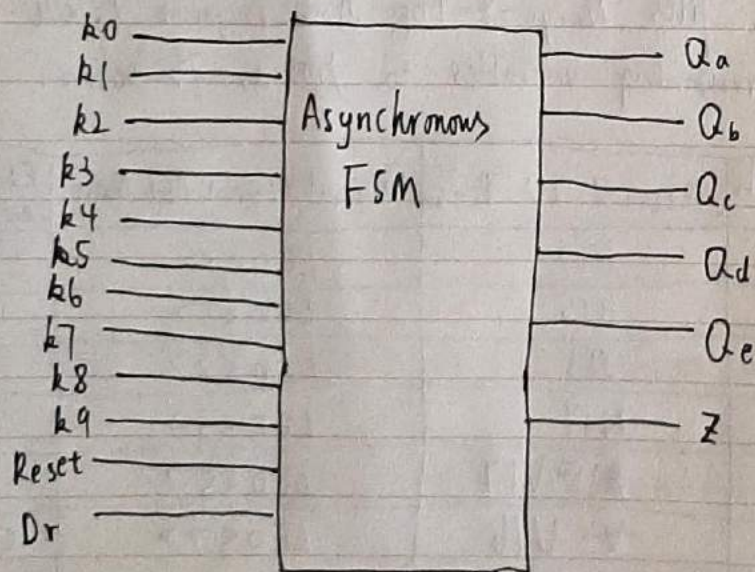

Editing the constraints files as below

(Output) Asynchronous FSM Signal	Artix I/O Pins	Original Digilent Net Name	Edited Digilent Net Name
Q _a	H17	LED <0>	Q _a
Q _b	K15	LED <1>	Q _b
Q _c	J13	LED <2>	Q _c
Q _d	N14	LED <3>	Q _d
Q _e	R18	LED <4>	Q _e
Z	U16	LED <7>	Z

(Input) Asynchronous FSM Signal	Artix I/O Pins	Original Digilent Net Name	Edited Digilent Net Name
k0	J15	SW <0>	k0
k1	L16	SW <1>	k1
k2	M13	SW <2>	k2
k3	R15	SW <3>	k3
k4	R17	SW <4>	k4
k5	T18	SW <5>	k5
k6	U18	SW <6>	k6
k7	R13	SW <7>	k7
k8	T8	SW <8>	k8
k9	V8	SW <9>	k9
Dr	T13	SW <11>	Dr
Reset	U12	SW <13>	Reset

Summary

- ① map names of variables and pins in the constraints files
- ② Ignore the combinational loop alert by adding
'see property ALLOW_COMBINATIONAL_LOOPS TRUE [get-nets]'
- ③ Wire ——— assign
reg ——— always
- ④ initial { sequential execution } ——— Test
always { parallel execution } ——— Design
- ⑤ Edit ~~src~~ source files properties,
clear 'implementation' and 'synthesis' for Test_Bench
- ⑥ Synchronous: clock
Asynchronous: race hazard